

Lesson 2: complex circuits – amplifiers – operational amplifier basics


Neurons are more than linear integrators. Their voltage-gates ion channels create complex dynamics.

To replicate neural dynamics with analog electronic circuits, we need a way to change the voltage of our sources during operation, using *controlled sources*.


A voltage controlled voltage source is the operational amplifier, short OA. Our neuron will use the MC6004 integrated operational amplifier.

KC4: MC6004 is an operational amplifier (OA).

It has an output V_{out} and two inputs $V_{noninverting}$ (short +) and $V_{inverting}$ (-).

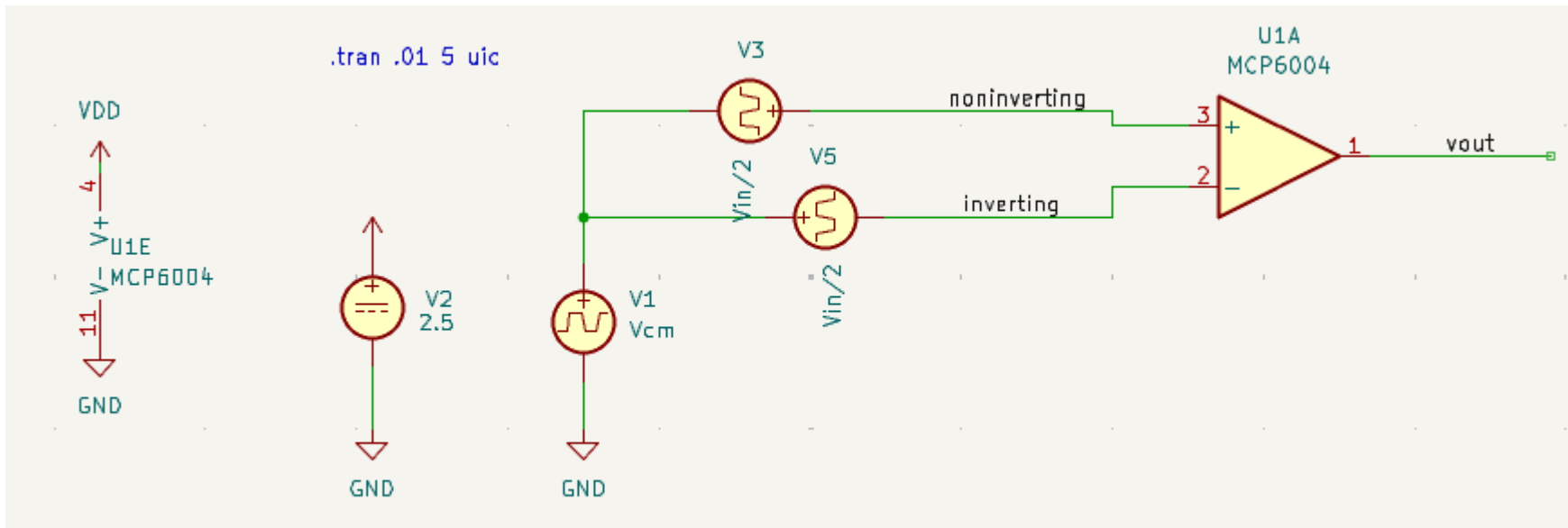

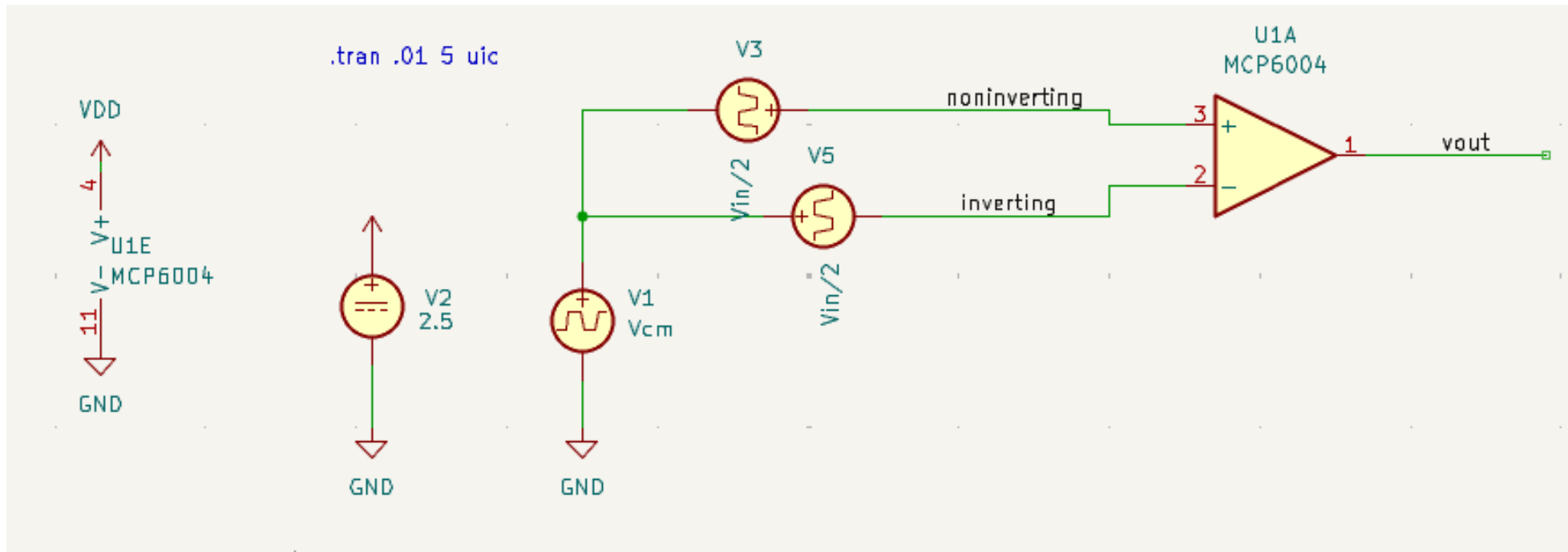Lesson 2: complex circuits – amplifiers – operational amplifier basics



Q4.1: Verify that it amplifies $V_{\text{noninverting}} - V_{\text{inverting}}$, i.e. $V_{\text{out}}(V_{\text{in}}) = A * (V_{\text{noninverting}} - V_{\text{inverting}})$. Determine A from the simulation.

technical hints:

- you have to copy the `/shares/zitipoolhome/nca-opt/models` directory to your KiCad directory (where your `.kicad_pro` and `.kicad_sch` files are)
- you may use `/shares/zitipoolhome/nca-opt/2_opamp_basic.kicad_pro` and `/shares/zitipoolhome/nca-opt/2_opamp_basic.kicad_sch`


Q4.2: Does it amplify V_{cm} ?

Lesson 2: complex circuits – amplifiers – feedback

KK5: try the following configurations for the amplifier.

Q5.1:
derive the three functions $V_{out}(V_{in})$.
Treat the Op like a voltage controlled ($V_+ - V_-$) ideal voltage source.

Hint:
Assume, that the amplification A of the OP is so high ($\sim 10^6$) that the difference between the two inputs is nearly zero whenever the output voltage is not gnd or vdd. Use this fact to answer the question, i.e. use $(V_+ - V_-) = 0$ and calculate $V_{out}(V_{in})$ using Kirchhoffs laws.
The input resistance of the + and – pins is so high that you can assume $I_+ = 0$ and $I_- = 0$.

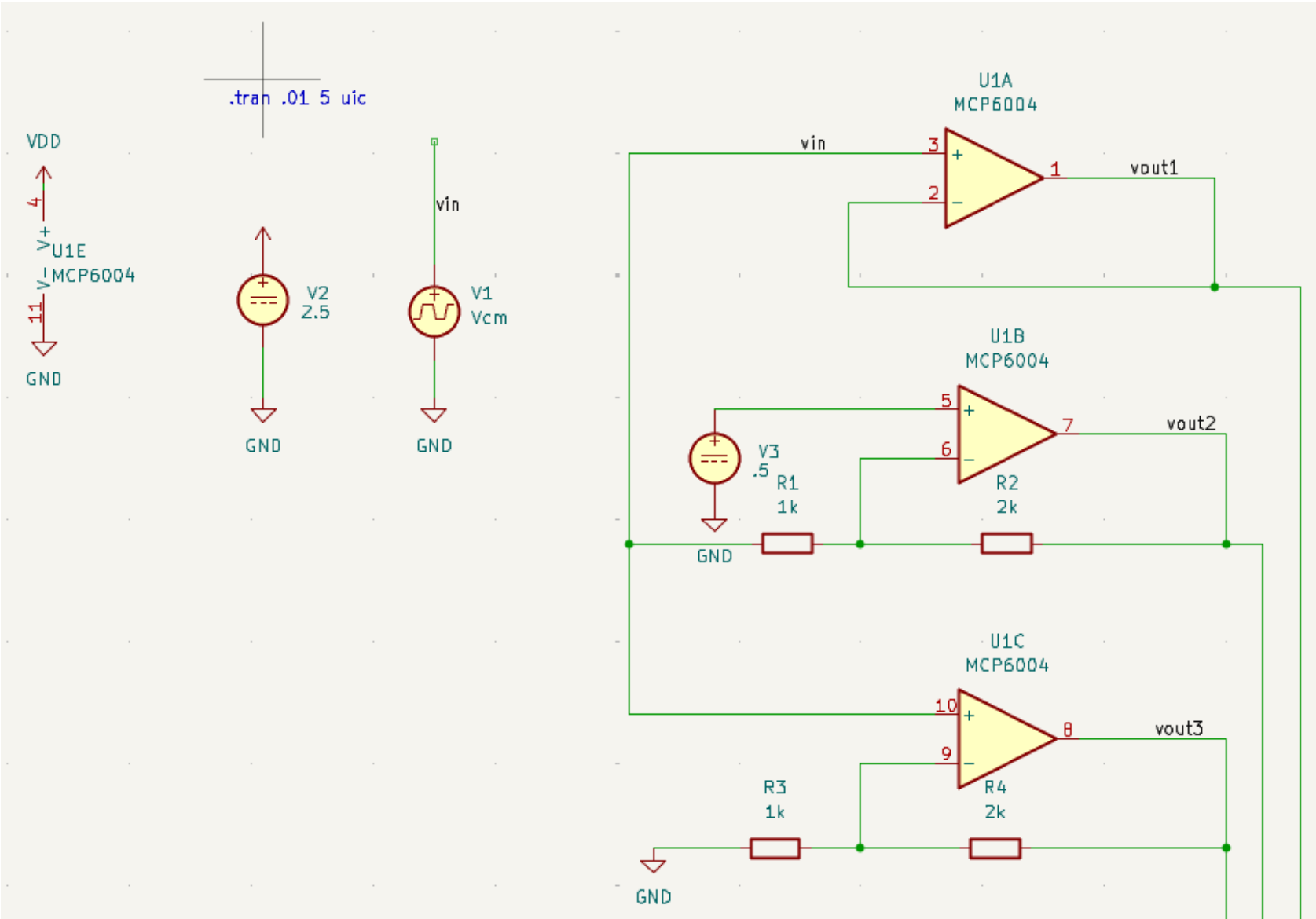

Lesson 2: complex circuits – amplifiers – adder circuit

KK6: the three output voltages are combined by resistors at the noninverting input of the U1D.

Q6.1: derive the function of the circuit and verify in simulation

